
# **LED Drivers for High-Brightness Lighting**

### Solutions Guide

national.com/LED

### 2010 Vol. 1

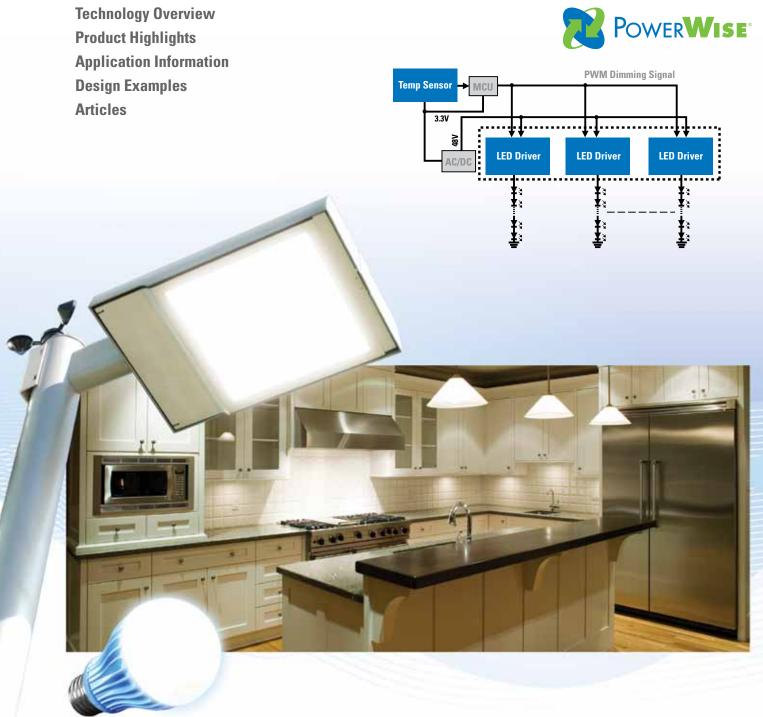



# **Energy-Efficient LED Driver Designs**

#### national.com/LED

or 50 years, National has been known for its reliable, energy-efficient power management products. The company continues to bring this knowledge, experience, and manufacturing capability to help customers create better lighting designs. National's LED drivers incorporate the intelligence that systems need to deliver high-performance, reliable, and robust LED lighting solutions to the market.

National Semiconductor's broad portfolio of PowerWise® energy-efficient power management ICs provide constant current for driving both low-power and high-brightness LEDs, enabling color and brightness matching over



a wide temperature range. These LED drivers enable greater energy efficiency and flexibility in lighting designs. Driving numerous LEDs in one string, they provide greater than 90 percent efficiency and

accurate current regulation with less power and heat dissipation.

#### **Solving Customer Design Challenges**

To enable customers to build differentiated products more quickly, National's easy-to-use solutions address a number of lighting design challenges through features such as:

- · Dynamic headroom control to maximize system efficiency
- Multiple outputs maximize LED strings per driver and reduce system solution size, cost, and complexity
- Thermal foldback ensures LEDs operate reliably over varying temperature conditions for a robust solution that doesn't require complex external temperature sensing circuitry
- Patent-pending architectures enable state-of-the-art TRIAC/ phase dimming compatibility in LED retrofit lamps and new installation fixtures for a seamless transition to LED lighting technology
- Analog and Pulse-Width Modulation (PWM) dimming capabilities for design flexibility
- Small driver solutions for space-constrained applications
- Tools such as WEBENCH® LED Designer for easier design

#### Award-Winning Design Tools

National's unique WEBENCH LED Designer online tool allows for quick and easy selection and simulation of a complete LED and LED driver solution. The tool



provides lighting designers a competitive advantage and faster time to market. National's on-demand tools make it easy for designers to explore and learn, compare and select products, and then design and build their system online.

#### Wide Range of Applications

**Replacement lamps** 

National has products that fit into a wide range of applications including:

• Downlighting



- Outdoor area fixtures such as street lamps and parking garage lights
- Industrial/commercial such as high bay and low bay fixtures for warehouse lighting
- · Portable consumer: flashlights and sports equipment
- Entertainment and projection
- Architectural/decorative fixtures
- LED backlit displays
- Automotive headlamps
- ... and more



### **Contents**

Fechnology Overview	4
ED Drivers Selection Tables	6
Key Product Overview	8
Applications	
Two-Wire Dimming	12
LED Bulbs	13
Outdoor High-Power Wide Area	18
Portable Projectors	22
Automotive	
TRIAC Dimming	28
Designer's Corner	29
Design Resources	33

#### **Overview**

Regardless of type, color, size, or power, all LEDs work best when driven with a constant current. LED manufacturers specify the characteristics (such as lumens, beam pattern, color) of their devices at a specified forward current ( $I_F$ ), not at a specific forward voltage ( $V_F$ ).

Most power supply ICs are designed to provide constant voltage outputs over a range of currents (see below); hence, it can be difficult to ascertain which parts will work for a given application from the device datasheet alone.

With an array of LEDs, the main challenge is to ensure every LED in the array is driven with the same current. Placing all the LEDs in a series string ensures that exactly the same current flows through each device.


# High-Brightness LEDs: Input Voltage and Forward Voltage

Sources of input voltage for LED arrays come from batteries or power supplies that have a certain tolerance. An automotive battery, for example, may supply 8V to 16V depending on the load and the age of the battery. The "silver box" power supply inside a desktop CPU may supply 12V  $\pm$ 10%.


High-brightness (HB) LEDs also give a range of forward voltage. A typical HB LED might be characterized at a forward current of 350 mA. The forward voltage of the LED when  $I_F = 350$  mA is specified with a range that includes a typical value as well as over-temperature maximum and minimum values. To ensure that a true constant current is delivered to each LED in an array, the power topology must be able to deliver an output voltage equal to the sum of the maximum forward voltages of every device placed in the string.

Manufacturers bin their devices for color, brightness, and forward voltage. Binning for all three characteristics is expensive, and forward voltage is often the specification that is allowed to vary the most. Adding this to the shift in forward voltage as the LED die temperature changes gives rise to the need for constant-current regulators that have a wide range of output voltage.

#### **Constant Voltage Regulator**

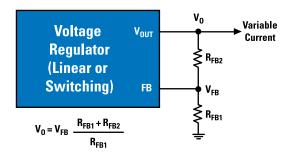

#### **Constant Current Regulator**

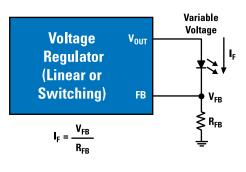

#### When Input Voltage Exceeds LED Voltage

If input voltage always exceeds the sum of the maximum forward voltages of every LED in a string, then two options are available: linear regulators and buck regulators.

A linear regulator introduces efficiency and thermal drawbacks, but is the simplest design option. In order to provide constant current, the linear regulator must be an adjustable type that uses a pair of feedback resistors. Replacing the top feedback resistor with the LED string and placing a current-sensing resistor in the bottom position "tricks" the former constant voltage source into adjusting the output voltage until enough current flows through the current sensing resistor to equal the feedback voltage of the IC.

Linear regulators have the advantages of simplicity, low parts count, and very little Electromagnetic Interference (EMI). They can deliver constant current as long as the V<sub>F</sub> in the LED string does not exceed their dropout-limited output voltage. The disadvantage lies in efficiency and thermal dissipation. Loss in a linear regulator LED driver is approximately equal to  $(V_{IN} - n \times V_F) \times I_F$ , where "n" is the number of LEDs in the string. At currents of 350 mA and above, the linear solution may require a heatsink, adding cost and size to the design.

The more efficient option when input voltage always exceeds the LED voltage is a step-down or buck regulator. As with linear regulators, this must be an adjustable type, and the same method can be used to turn almost any buck regulator into a constant current source for LEDs. Buck regulators enjoy high efficiency and eliminate the need for a heatsink, at the cost of a more complex circuit and the addition of switching noise. Many recent buck regulators switch at 1 MHz and above, making their external components so small that at currents under 1A they may actually use less space than a linear regulator.

# When Input Voltage is Less than LED Voltage

When the minimum forward voltage of all the LEDs in a string will always exceed the maximum input voltage, a step-up, or boost, regulator is needed.

The inductive-boost converter is the simplest regulator that can deliver currents above 350 mA with a varying output voltage. As with linear and buck regulators, a boost converter with a feedback-divider network can be modified to become a constant current source. One important distinction between the buck regulator and boost regulator must be made when the power switch is internal to the control IC. Such monolithic systems have a fixed current limit.

In buck regulators, the internal switch passes the same DC current as the LED. A boost converter differs in that the internal switch sees a higher current that varies with input voltage; the greater the difference between V<sub>IN</sub> and V<sub>OUT</sub>, the higher the internal switch current. Care must be taken to evaluate a monolithic boost regulator-based LED drive to make sure that it will not hit the fixed current limit over the range of input voltage.

# When Input Voltage Range Overlaps LED Voltage Range

As HB LEDs are adopted into more and more applications, situations will arise when the input voltage varies above and below the forward voltage of the LED string. For these cases, a current regulator is needed that can both buck and boost as required by the input and output conditions. Possible topologies include the buck-boost, SEPIC, Cuk, flyback, and  $V_{\rm IN}$  referenced buck-boost (also called the floating buck-boost).

In all of these topologies, the power-switch current exceeds the LED current and varies with input voltage. The same attention to peak switch current must be made over the full range of input voltage, especially if a regulator with an internal power switch and fixed current limit is implemented. For more information about National's LED products, samples, design simulation tools, and more, visit: national.com/LED.

#### **Buck (Step-down) High-Brightness LED Drivers**

Product ID		V <sub>IN</sub> Range (V)	ν <sub>ουτ</sub> (ν)	I <sub>LED</sub> (A)	No. of LED	Internal SWITCH	Topology	Key Features	Auto Grade
LM3401 E, W	R	4.5 to 35	Up to 35	3	1 to 9	_	Buck	Dual-side hysteresis, very low reference voltage and short propagation delay, 100% duty cycle	
LM3402/HV E, W	R	6.0 to 42/6.0 to 75	Up to 37/67	0.425	1 to 9/15	~	Buck	200 mV feedback voltage, fast PWM dimming	
LM3404/HV E, W	R	6.0 to 42/6.0 to 75	Up to 37/67	1	1 to 9/15	~	Buck	200 mV feedback voltage, fast PWM dimming	
LM3405A E, W	R	3.0 to 22	Up to 20	1	1 to 3	~	Buck	200 mV feedback voltage, fast PWM dimming, thin package	
LM3406/HV E, W	R	6.0 to 42/6.0 to 75	Up to 37/67	1.5	1 to 9/15	~	Buck	200 mV feedback voltage, fast PWM or two-wire dimming, true average current control	
LM3407 <sup>E, W</sup>	R	4.5 to 30	Up to 27	0.35	1 to 7	~	Floating Buck	Constant frequency PWM with true average current control	
<b>LM3409/HV</b> E, W	R	6.0 to 42/6.0 to 75	Up to 42/75	3.0+	1 to 9/15	_	Buck	External high-side P-FET current source with differential current sensing and analog current adjust, 100% duty cycle	-
LM3414/HV E, W (	R	4.5 to 65	Up to 60	1	1 to 15	~	Floating Buck	Requires no external current sensing resistor and no external compensation, LED current adjustment, temperature foldback	
LM3421 <sup>E, W</sup>	R	4.5 to 75	Adjustable	3.0+	1 to 16	_	Floating Buck	20 mV to 1.235V adjustable differential current sense voltage, 50 kHz max PWM dimming	<b>a</b>
LM3423 E, W	R	4.5 to 75	Adjustable	3.0+	1 to 16	_	Floating Buck	20 mV to 1.235V adjustable differential current sense voltage, 50 kHz max PWM dimming, fault timer, LED ready flag, high-side dimming	=
LM3424 <sup>E, W</sup>	R	4.5 to 75	Adjustable	3.0+	1 to 18	_	Floating Buck	Temperature foldback, synchronizable 50 kHz max PWM dimming	<b>a</b>
<b>LM3429</b> E, W	R	4.5 to 75	Adjustable	3.0+	1 to 20	_	Floating Buck	50 mV to 1:25 adjustable high-side current-sense voltage, analog and PWM dimming	=
LM3433 E, W	R	-9.0 to -14	Up to 6	20+	1 to 2	_	Negative SYNC Buck	Negative output voltage capability allows LED anode to be tied directly to chassis for max heat sink efficacy	
<b>LM3434</b> E, W	R	-9.0 to -30	Up to 27	20+	1 to 6	_	Negative SYNC Buck	Output current > 20A, PWM frequency capable > 30 kHz, negative output voltage capability allows LED anode to be tied directly to chassis for maximum heat sink efficacy	

#### **Dynamic Headroom Control (DHC) High-Brightness LED Driver Solutions**

	Product ID	V <sub>IN</sub> Range (V)	V <sub>out</sub> (V)	I <sub>LED</sub> (A)	No. of LED	Multi- Output	Internal SWITCH	Topology	Key Features
NEW	LM3464 E 🕱	12 to 80	Adjustable to 79	3.0+	20 per ch	4 ch		Individual Current Regulator + DHC	4-channels with individual current regulation, DHC output interfaces with external power supply to adjust LED supply voltage for maximum efficiency, temperature foldback, analog and PWM dimming

Z PowerWise® product E Evaluation board W WEBENCH enabled

Product ID	V <sub>IN</sub> Range (V)	V <sub>out</sub> (V)	I <sub>LED</sub> (A)	No. of LED	Multi- Output	Internal SWITCH	Topology	Key Features	Auto Grade
LM3410 E. W 🔊	2.7 to 5.5	24	2.1(1)	1 to 5	—	~	Boost	Ultra-low stand-by current of 80 nA, internally compensated	=
LM3421 E. W 🔊	4.5 to 75	Adjustable	3.0+	1 to 20	_	_	Boost	20 mV to 1.235V adjustable differential current sense voltage, 50 kHz max PWM dimming	<b>a</b>
LM3423 E, W 🕱	4.5 to 75	Adjustable	3.0+	1 to 20	_	_	Boost	20 mV to 1.235V adjustable differential current sense voltage, 50 kHz max PWM dimming, fault timer, LED ready flag, high-side dimming	=
LM3424 E. W 🎗	4.5 to 75	Adjustable	3.0+	1 to 18	—	_	Boost	Temperature foldback, synchronizable 50 kHz max PWM dimming	<b>a</b>
LM3429 E. W 🎘	4.5 to 75	Adjustable	3.0+	1 to 20	_	_	Boost	50 mV to 1:25 adjustable high-side current-sense voltage, analog and PWM dimming	<b>a</b>
LM3431 E, W 🎗	5.0 to 36	40	0.15	3 x 10	~	—	Boost	LED protection: short, open, and thermal	

#### **Boost (Step-up) High-Brightness LED Drivers**

#### **Buck-Boost High-Brightness LED Drivers**

Product ID	V <sub>iN</sub> Range (V)	V <sub>out</sub> (V)	I <sub>LED</sub> (A)	No. of LED	Multi- Output	Internal SWITCH	Topology	Key Features	Auto Grade
LM3410 E, W 🔊	2.7 to 5.5	24	2.1 <sup>(1)</sup>	1 to 5	—	~	SEPIC	Ultra-low stand-by current of 80 nA, internally compensated	<b>a</b>
LM3421 E, W 🔀	4.5 to 75	Adjustable	3.0+	1 to 20	_	_	Floating Buck- Boost SEPIC	20 mV to 1.235V adjustable differential current sense voltage, 50 kHz max PWM dimming	<b>a</b>
LM3423 E, W	4.5 to 75	Adjustable	3.0+	1 to 20	_	_	Floating Buck- Boost SEPIC	20 mV to 1.235V adjustable differential current sense voltage, 50 kHz max PWM dimming, fault timer, LED ready flag, high-side dimming	<b>a</b>
LM3424 E, W 🔊	4.5 to 75	Adjustable	3.0+	1 to 18	_	—	Floating Buck- Boost SEPIC	Temperature foldback, synchronizable 50 kHz max PWM dimming	<b>a</b>
LM3429 E, W 🔊	4.5 to 75	Adjustable	3.0+	1 to 20	_	_	Buck-Boost Flyback SEPIC	50 mV to 1:25 adjustable high-side current-sense voltage, analog and PWM dimming	<b>a</b>

#### **Offline High-Brightness LED Driver Solutions**

Product ID	V <sub>IN</sub> Range (V)	V <sub>out</sub> Max (V)	I <sub>LED</sub> (A)	No. of LED	Multi-Output	Internal SWITCH	Topology	Key Features
LM3445 E, W 🏼 🏧	80 to 270	Adjustable	1+	1 to 14+	_	_	Floating Buck	Integrated TRIAC dim decoder circuit for LED dimming, adaptive programmable offline allows for constant ripple current, no 120/100 Hz flicker

Note (1) Specified in ISW Z PowerWise® product <sup>E</sup> Evaluation board <sup>W</sup>WEBENCH enabled


#### LM3464 – PowerWise® LED Driver with Dynamic Headroom Control

#### **Theory of Operation**

- Four individual current regulator channels work in conjunction with external N-channel MOSFETs and sense resistors to accurately drive current for every LED string
- Dynamic Headroom Control (DHC) output interfaces with an external power supply to adjust LED supply voltage to the lowest level adequate to maintain all string currents in regulation, yielding maximized efficiency and reduced system complexity
- Digital Pulse-Width Modulation (PWM)/analog dimming control interface provides thermal foldback and increases system reliability
- Protection features include wide input voltage range (12V to 80V), Under-Voltage Lockout (UVLO), LED open/short circuit, and over-temperature fault signal to the system controller
- Available in eTSSOP-28 packaging
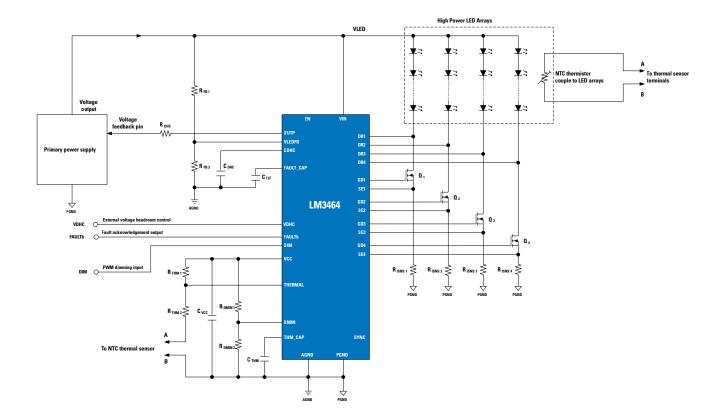
#### Applications

Ideal for solid-state lighting solutions or multi-string, white light applications such as street lights, high bay/warehouse lighting, automotive headlamps, and office troffers



#### **Typical Application Circuit**


#### LM3421/23/24/29 – PowerWise® N-Channel Controllers for Constant-Current LED Drivers

#### **Theory of Operation**

- Versatile high-voltage LED driver controllers can be configured in buck, boost, buck-boost (flyback), or SEPIC topologies
- Designed for adjustable-switching frequencies of up to 2.0 MHz
- Fast PWM dimming, cycle-by-cycle current limit, over-voltage protection, and input under-voltage protection
- LM3424 includes an integrated thermal foldback feature to provide a more robust thermal design to extend the life of the LED and increase system reliability
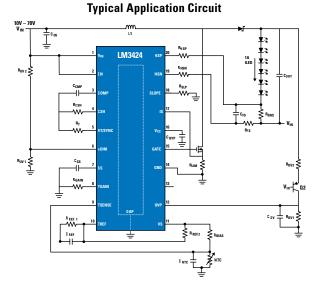
#### Applications

Ideal for illuminating LEDs in a very diverse, large family of applications



#### LM3414/14HV – PowerWise® 1A, 60W Common-Anode-Capable, Constant-Current Buck LED Driver


#### **Theory of Operation**

- Wide input voltage range (4.5V to 65V)
- Requires no external current sensing resistor and no external compensation, enabling a more compact and simpler solution
- · Common-anode capable for minimum wiring
- LED current adjustment (350 mA to 1000 mA) enables precise LED current settings
- Analog dimming and thermal foldback provide a more robust and versatile system
- Supports all-ceramic capacitors

- Pulse-Level Modulation (PLM) control reduces power loss benefitting in high conversion efficiency and true average LED current regulation
- Adjustable constant switching frequency (100 kHz to 1000 kHz), thermal shutdown protection, and  $V_{cc}$  UVLO
- Available in power-enhanced PSOP-8 or LLP-8 packaging (3 x 3 mm)
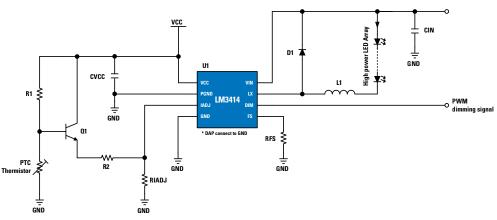
#### **Applications**

Ideal for illuminating LEDs in a very diverse, large family of applications, especially space-constrained applications such as MR16 bulbs



#### **Typical Application Circuit**

national.com/LED

#### LM3409/09HV – PowerWise® PFET Buck Controller for High-Power LED Drivers

#### **Theory of Operation**

- P-channel MOSFET (PFET) controllers for step-down (buck) current regulators
- · Wide-input voltage range, high-side differential current sense with low adjustable threshold voltage, fast-output enable/ disable function
- Constant Off-Time (COFT) control regulates an accurate constant current without the need for external control-loop compensation
- · Analog and PWM dimming are easy to implement and result in a highly linear dimming range with excellent achievable contrast ratios
- UVLO, low-power shutdown, and thermal shutdown
- Can drive LEDs at currents >3A ٠
- Available in eMSOP-10 packaging

#### **Applications**

Ideal for illuminating LEDs in a very diverse, large family of applications

#### LM3445 – PowerWise® TRIAC Dimmable Offline LED Driver


#### **Theory of Operation**

Conventional TRIAC dimmers are designed to interface to a resistive load (halogen or incandescent bulb), while today's LED driver solutions interfaced to a standard wall dimmer produce 120 Hz flicker of the LED and/or do not allow 100:1 dimming.


- LM3445 LED driver decodes the TRIAC chopped waveform and translates the signal to dim the LEDs, achieving a full, wide dimming range without flicker
- Best-in-class dimming performance
- High efficiency
- Maintains ENERGY STAR<sup>®</sup> power factor requirements in a ٠ typical application

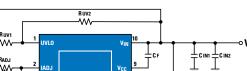
#### **Applications**

Ideal for any application where an LED driver must interface to a standard TRIAC wall dimmer



**Typical Application Circuit** 

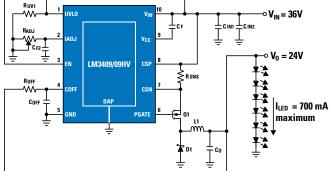

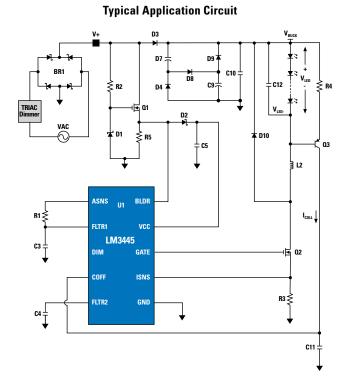

### National Offers a Diverse Portfolio of Constant-Current Regulators for Driving LEDs

#### **Applications**

LED Driver	LED Bulbs	Outdoor High-Power Wide Area	Indoor/Downlight Fixtures	Automotive	Display Backlighting	Medical	Entertainment	Portable Consumer	Projectors
LM3401	~	<i>v</i>	~	~		~	~	~	
LM3402/HV	~	~	~	~		~	~		
LM3404/HV	~	~	~	~		~	~		
LM3405/A	~	~	~	~		~		~	
LM3406/HV	~	~	~	~		~	~		
LM3407	~	~	~	~		~		~	
LM3409/HV	~	~	~	~		~	~		
LM3410	~			~	~	~		~	
LM3414	~	~	~	~		~	~	~	
LM3421/23	~	~	~	~	~	~	~		
LM3424	~	~	~	~		~	~		
LM3429	~	~	~	~		~	~	~	
LM3430/32				~	~	~			
LM3431				~	~	~			
LM3433						~	~		~
LM3434						~	~		~
LM3445	~								
LM3464		~	~	~		~			

### **High-Brightness LED Applications**


Two-Wire Dimming

#### **Two-Wire Dimming**
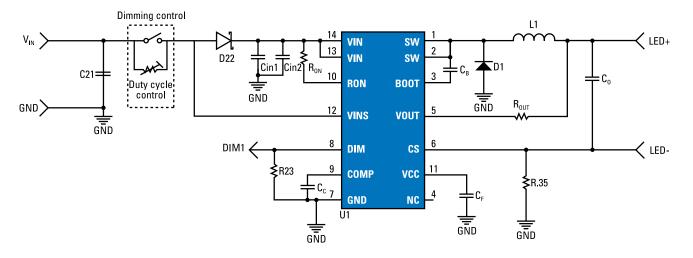
#### LM3406 Two-Wire Dimming

Adding an external input diode and using the internal  $V_{\rm INS}$  comparator allows the LM3406/06HV to sense and provide PWM dimming of the LED by chopping of the input voltage. This method is also referred to as "two-wire dimming," and a typical application circuit is shown below.

If the V<sub>INS</sub> pin voltage falls 70% below the V<sub>IN</sub> pin voltage, the LM3406/06HV disables the internal power FET and shuts off the current to the LED array. The support circuitry (driver, bandgap, V<sub>CC</sub>) remains active in order to minimize the time needed to turn the LED back on when the V<sub>INS</sub> pin voltage rises and exceeds 70% of V<sub>IN</sub>. This minimizes the response time for turning the LED array back on.




The benefit of two-wire dimming: One wire less than traditional PWM dimming, further reducing the wiring cost

## High-Brightness LED Applications LED Bulbs

#### **MR16**

#### **MR16 Basic Architecture**

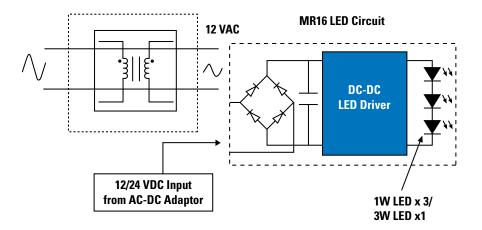


#### **MR16 Driver Solutions**

V <sub>IN</sub>	No. of LEDs	LED Type (W)	I <sub>LED</sub> (mA)	Recommended Part No.	Key Features
12 to 24 VAC-VDC	1 to 3	1 to 5	>1	LM3421/29	Buck-boost architecture
12 to 24 VAC-VDC	1 to 3	1 to 5	>1	LM3424	Buck-boost architecture, thermal foldback
12 to 48 VDC	1	5	350	LM3406	Two-wire dimming, high efficiency
12 to 24 VDC	3	1	350	LM3401	100% duty cycle
12 to 48V	3	5	350	LM3409	100% duty cycle, analog dimming
12 VAC	3	1	350	LM3414	100% duty cycle, analog dimming
12 VDC/12 VAC	3	1	350	LM3405A XMK	Small size, tiny SOT23-6 packaging
12 to 24 VDC	3	1	350	LM3407	High efficiency, high precision of LED current
12 VDC/12 VAC	1	3	600	LM3405A XMK	Small size, tiny SOT23-6 packaging
12 VDC/12 VAC	1	3	750	LM3405A XMY	Thermally enhanced package, eMSOP-8

#### Design 1: MR16 Using LM3405A
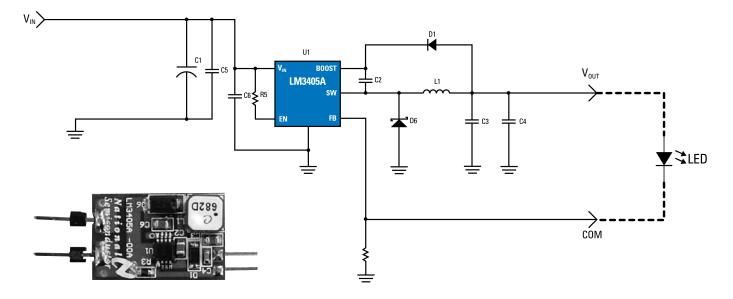
#### **Description:**

• This circuit is designed to drive a 3W high-brightness LED from an input of 12 VDC/12 VAC for halogen MR16 lamp replacement applications.



#### Test Data:

#### 1: Output Voltage & Current

Para	meter	Reading		
V <sub>IN</sub>	Load	V <sub>OUT</sub>	I <sub>LED</sub>	
12 VDC	1 LED	3.8V	0.70A	

#### 2: Efficiency


	Reading						
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency		
12V	12V	0.274A	3.80V	0.70A	80.9%		


Item	Designation	Description	Part No.	Vendor
1	U1	LED driver IC	LM3405A (eMSOP-8)	National
2	C1	16V, 220 μF, 8 x 7 mm	SG or YK, 220 μF, 16V	Lelon or Rubycon
3	L1	Inductor 6.8 μH, 0.095 Ω, 2.6A	LPS6225-682MLB	Coilcraft
4	Co	CAP0805, 0.47 μF	GRM188R71C474KA88	Murata

#### Design 2: MR16 Using LM3407
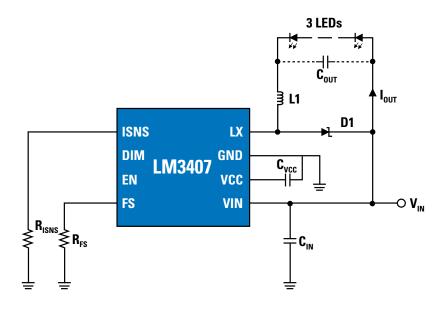
#### **Description:**

• This circuit is designed to drive an array of 3 series-connected 1W LEDs from an input of 12 VDC/12 VAC for MR16 lamp replacement applications.



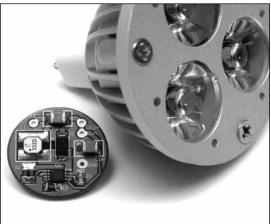

#### **Test Data:**

#### 1: Output Voltage & Current

Para	meter	Reading		
V <sub>IN</sub>	Load	V <sub>out</sub>	I <sub>LED</sub>	
12 VDC	3 LEDs	9.71V	0.35A	

#### 2: Efficiency


	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency
12V	12.01V	0.30A	9.71V	0.35A	94.06%

Item	Designation	Description	Part No.	Vendor
1	U1	LED driver IC	LM3407 (eMSOP-8)	National
2	L1	Inductor 33 µH, 0.58A	LPS-4018-333ML	Coilcraft
3	C <sub>IN</sub>	Cap MLCC 50V, 4.7 μF, X7R	GRM32ER71H475K88L	Murata
4	C <sub>OUT</sub>	Cap MLCC 25V, 2.2 μF, X7R	GRM31MR71E225MA93	Murata

#### Design 3: MR16 with Two-Wire Dimming Driven by the LM3406
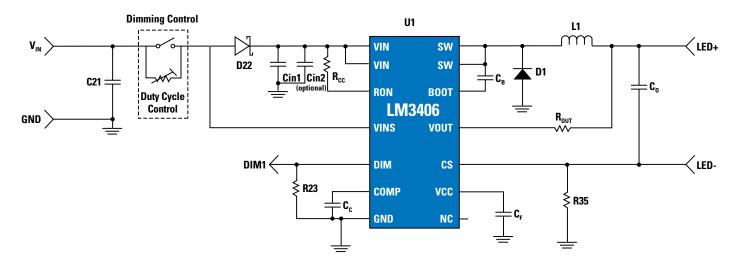
#### **Description:**

- This circuit is designed to drive a 1.5A high-brightness LED from an input of 12 VDC for MR16 lamp replacement applications.
- The two-wire dimming feature of LM3406 enables PWM dimming over the power input line.



#### **Test Data:**

#### **1: Output Voltage and Current**

Parameter		Reading	
V <sub>IN</sub>	Load	V <sub>out</sub>	I <sub>LED</sub>
12 VDC	2 LEDs	4.20V	1.50A

#### 2: Efficiency


	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency
12V	12V	0.62A	4.20V	1.50A	84.68%

Item	Designation	Description	Part No.	Vendor
1	U1	LED driver IC	LM3406 (eTSSOP-14)	National
2	L1	15 μH, 2.2A, 47 mΩ	SLF10145T-150M2R2-P	ТDК
3	Cin1	3.3 μF, 50V	C3225X7R1H335M	ТDК
4	Co	0.15 μF, 50V	C3216X7R1H105M	TDK

#### **OR111, PAR30 and PAR38**
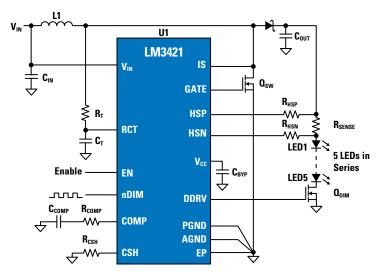
#### **Description:**

- This circuit is designed to drive an array of 5 to 8 seriesconnected 3W LEDs from an input of 12 VDC/12 VAC for existing QR111, PAR30/38 luminaire form factors.
- Since the total forward voltage of the LED string is higher than the input voltage, LM3421 is configured in a boost topology.



#### **Test Data:**

#### 1: Output Voltage & Current

Parameter		Reading	
V <sub>IN</sub>	Load	V <sub>OUT</sub>	I <sub>LED</sub>
12 VDC	5 LEDs	19.98V	0.72A

#### 2: Efficiency

	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency
12V	12V	1.27A	19.98V	0.72A	94.50%

ltem	Designation	Description	Part No.	Vendor
1	U1	Low-side controller for constant-current LED drivers	LM3421 (eTSSOP-16)	National
2	LI	15 μH	7447709150	Coilcraft
3	C <sub>IN</sub>	150 μF/50V	Aluminum eletrolytic capacitor, EEEFK1H151P	Panasonic
4	C <sub>OUT</sub>	150 μF/50V	Aluminum eletrolytic capacitor, EEEFK1H151P	Murata


### **High-Brightness LED Applications**

**Outdoor High-Power Wide Area** 

#### **48V Bus Street Lamp**
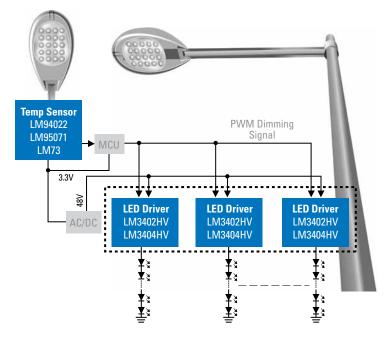
#### Key Benefits of LM3402/4/6HV in 48V (or higher) Bus LED Street Lamp System

- Wide input voltage range (6V to 42V) or (6V to 75V)
  Maximizes the number of LEDs per string (~10 to 12 LEDs in series for 1 LED driver)
  - Lower system solution cost
- Ultra-high-efficiency LED driving solution
  - 96% + efficiency with 10 LEDs connected in series
  - Enhanced thermal performance in the harsh street lamp working environment
- No compensation required
  Easy to use




**LED Street Lamp Architecture** 

#### LM3424 with Integrated Temperature Management

- Temperature foldback
  - Eliminates the need for external thermal management circuitry
  - Increases LED lifetime, allowing for a more robust and reliable system solution
  - WEBENCH<sup>®</sup> LED Designer online tool with thermal management feature available to implement temperature foldback
    - Ease of design on a system level
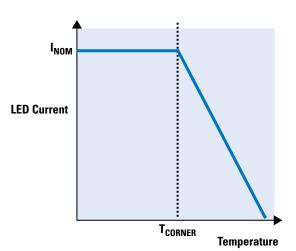
#### The Concept:

The thermal foldback feature lowers regulated current as the temperature increases to optimize the LED lifetime. The feature includes two parameters: A temperature corner (Tcorner) after which the nominal operating current is reduced and the slope corresponding to the amount of LED current decreases per temperature. The LM3424 allows the user to program both the breakpoint and slope of the thermal foldback profile using external resistors.




#### **Street Lamp**

#### Design 1: 1W LED String Using LM3402HV
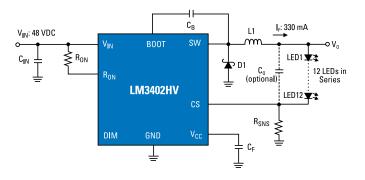
#### **Description:**

- This circuit is designed to drive an array of 10 to 12 seriesconnected 1W LEDs from a 48 VDC source.
- Multiple LM3402HV LED drivers can be used in the system, depending on the street lamp's output wattage.
- Each LM3402HV LED driver provides constant current for a single LED string. This enables consistent brightness of each LED in the LED street lamp.



#### **Test Data:**

#### 1: Output Voltage & Current

Parameter		Reading	
V <sub>IN</sub>	Load	V <sub>out</sub>	I <sub>LED</sub>
48 VDC	12 LEDs	38.20V	0.33A

#### 2: Efficiency

	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency
48V	47.91V	0.27A	38.20V	0.33A	98.04%

ltem	Designation	Description	Part No.	Vendor
1	U1	75V, 0.5A LED driver IC	LM3402HV (SOIC-8 or PSOP-8)	National
2	L1	18.5 x 15.4 x 7.1 mm 330 μH, 1.9A, 0.56Ω	D05022P-334	Coilcraft
3	Cin	2.2 μF/100V/1812	C4532X7R2A225M	ток
4	Co	0.15 μF, 100V, 1206	C3216X7R2A154M	ТDК


### **High-Brightness LED Applications**

**Outdoor High-Power Wide Area** 

#### Design 2: 3W LED String Using LM3404HV
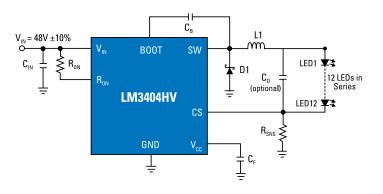
#### **Description:**

- This circuit is designed to drive an array of 10 to 12 seriesconnected 3W LEDs from a 48 VDC source.
- Multiple LM3404HV LED drivers are used in the LED street lamp system, depending on the street lamp's output wattage.
- Each LM3404HV LED driver provides constant current for a single LED string. This guarantees consistent brightness of each LED in the LED street lamp.



#### Test Data:

#### 1: Output Voltage & Current

Parameter		Reading	
V <sub>IN</sub>	Load	V <sub>OUT</sub>	I <sub>LED</sub>
52 VDC	12 LEDs	41.975V	1.071A

#### 2: Efficiency


	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	ILED	Efficiency
52V	51.97V	0.847A	41.975V	1.017A	96.97%

ltem	Designation	Description	Part No.	Vendor
1	U1	75V, 1.2A LED driver	LM3404HV (SOIC-8 or PSOP-8)	National
2	L1	Inductor 220 μH, 0.229Ω, 2.2A	MSS1278-184KL	Coilcraft
3	Cin	2.2 μF/100V/1812	C4532X7R2A225M	ток
4	Co	0.15 μF, 100V, 1206	C3216X7R2A154M	ТДК

### **EMI Design for LED Street Lamp Application**

The LM3402HV circuitry shown in *Figure 1* is based on a street lamp application. The input is 48 VDC and the output is 12 seriesconnected 1W LEDs. To address the EMI concerns, the schematic and PCB layout were modified. As a result of the modifications, as shown in *Figure 2* below, better EMI performance was achieved and the design passed the EN55022 standard. The modifications are:

- One resistor Rz (50 Ω) is added between the SW pin and Cb pin. This changes the SW node waveform from *Figure 3* to *Figure 4*. The criterion of Rz selection is dependent on the SW turn-on slew rate and its ringing. The smaller the ringing, the better.
- 2: 1 µF output cap is added across LED connection port.
- 3: Input loop area should be kept as small as possible, which is shown in the blue-dashed area of *Figure 5*. C<sub>IN</sub> should be connected with the anode of catch diode directly.
- 4: The SW node should be kept as short as possible.

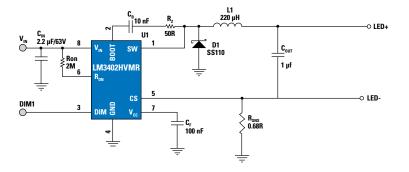




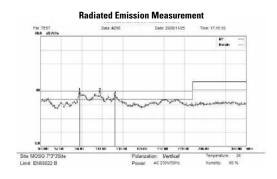


Figure 2

Pulsating Current High dv/dt node

L.

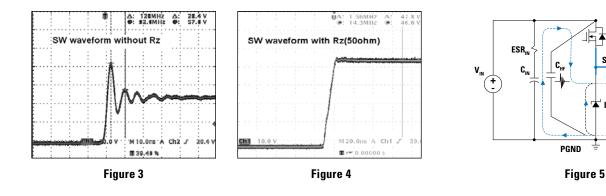


### **High-Brightness LED Applications**

### **Portable Projectors**
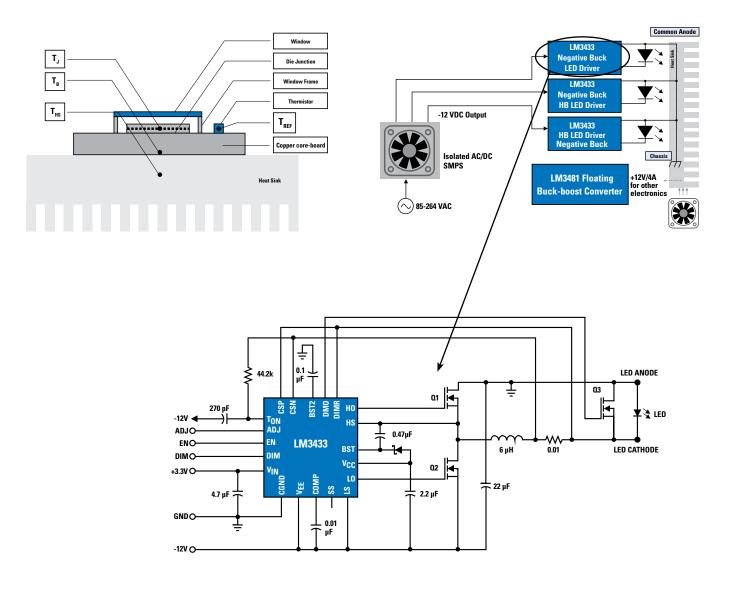
#### **Portable Projector**


- The LM3433/34 is a high-power constant-current LED driver controller which employs a negative synchronous buck topology, making it ideal for applications where a commonanode LED system is used for high current output.
- An example power architecture of a portable projector using the LM3433 is shown below. The -12 VDC isolated AC/DC SMPS is used for powering LM3433 LED drivers while the LM3481 floating buck-boost is used to generate positive outputs for other logic and interface.



#### LED Projector Using LM3433/34
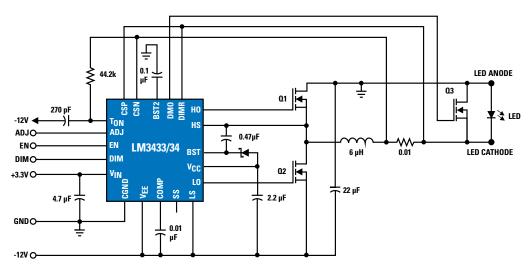
#### **Description:**

- This circuit is designed to drive a high-brightness commonanode LED module from a -12 VDC source (LM3433) or -20 VDC source (LM3434).
- In LED-based portable projector systems, green, blue, and red high-brightness common-anode LED modules are used as light sources. Each color requires one LM3433/34 driver.



#### **Typical Application Circuit**

#### **Test Data:**

#### **1: Output Voltage and Current**

2: Efficiency

	Parameter	Reading			Reading					
V <sub>IN</sub>	Load	V <sub>OUT</sub>	I <sub>LED</sub>		Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	Vout	I <sub>LED</sub>	Efficiency
-12 VDC	1 LED	4.60V	6A		-12V	-12V	2.47A	-4.60V	6A	93%

#### **BOM (Main Components)**

ltem	Designation	Description	Part No.	Vendor
1	U1	Common-anode-capable high-brightness LED driver with high-frequency dimming	LM3433 (LLP-24)	National
2	L2	12 μΗ, 14Α	GA3252-AL	Coilcraft
3	C3	150 μF, 16V	16SA150M	MULTICAP
4	C4	1210 22 μF x 2, 16V	GRM32ER61C226KE20L	Murata
5	C6	1210 47 μF, 16V	GRM32ER61C476ME15L	Murata
6	MOSFET (01,02,03,04)	PowerPAK 30V, 9.5 mΩ	Si7386DP	Vishay
7	LED	6A	PT39	Luminus


#### national.com/LED

## **High-Brightness LED Applications**

Automotive Lighting

From headlights to LCD backlighting in infotainment systems, LEDs are an integral part of the driving experience. National's portfolio of LED drivers offers key features like PWM dimming, accurate UVLO, and high-side current sensing. Plus, low LED ripple current and external oscillator sync capabilities allow designers to reduce issues with EMI. These LED drivers provide maximum efficiency and effectiveness in any automotive lighting system.

Features	Benefits
High efficiency	Better thermal management
High-side current sensing	LEDs grounded to chassis for better thermal dissipation
Accurate current control	Extends LED lifetime
PWM and analog dimming	Easily reduces current when battery is low to avoid excessive battery drain
Wide voltage range	Stable under instant on, low and high battery, high voltage transients
External oscillator sync capability	External spread spectrum for low EMI

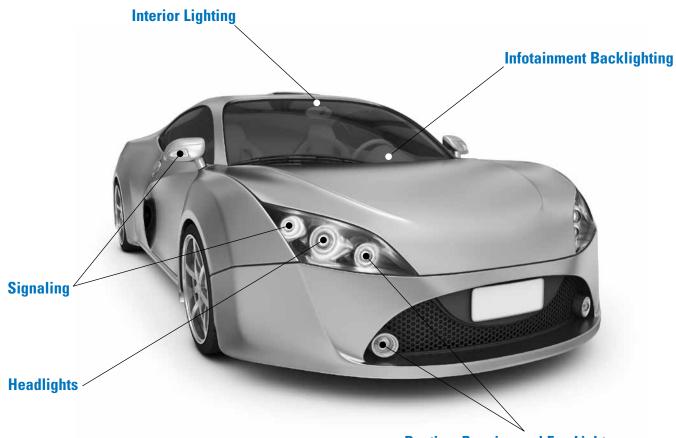



**Daytime Running and Fog Lights** 

#### Design 1: Driving Daytime Running Lamp (DRL) with LM3423 Boost LED Driver
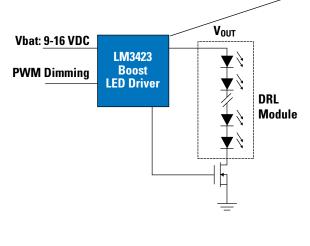
#### **Description:**

- This circuit is designed to drive a single string of 12 seriesconnected 1W LEDs from the battery input for daytime running lamps (DRL) in passenger cars.
- Since the total forward voltage of the LED string is higher than the battery input voltage, a boost (step-up) LED driver is required.



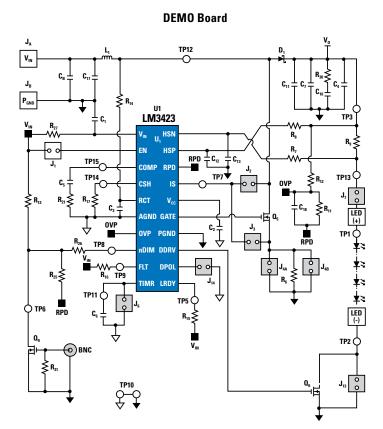

#### Test Data:

#### 1: Output Voltage & Current

Parameter		Reading		
V <sub>IN</sub>	Load	V <sub>OUT</sub>	I <sub>LED</sub>	
12 VDC	12 series-connected 1W LEDs	46V	0.40A	

#### 2: Efficiency

	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency
12V	12V	1.65A	46V	0.40A	92.93%

#### **BOM (Main Components)**

ltem	Designation	Description	Part No.	Vendor
1	U1	Low-side controller for constant-current LED drivers	LM3423 (eTSSOP-20)	National
2	L1	22 μH	D05040H	Coilcraft
3	C8 (Cin)	330 μF, 35V 5 mm	ECA-1VM331	Panasonic
4	C7 (Cout1)	330 μF, 35V 5 mm	ECA-1VM331	Panasonic
5	C11 (Cout2)	1210 10 µF, 25V	ECJ-4YB1E106M	Panasonic


#### national.com/LED


### Automotive Lighting

#### Design 2: Headlamp Using LM3423 Buck-Boost LED Driver
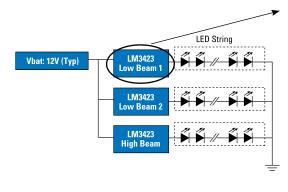
#### **Description:**

- This circuit is designed to drive a single string of 6 seriesconnected 3W LEDs from both a 12V and a 24V bus battery input for automotive headlamp applications.
- Since the total forward voltage drop of the LED string can be either higher or lower than the input voltage, a buck-boost LED driver is required.



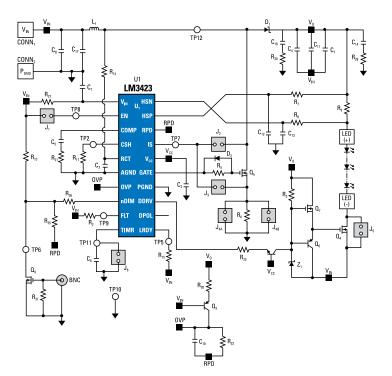

#### Test Data:

#### 1: Output Voltage & Current

Parameter		Reading		
V <sub>IN</sub>	Load	V <sub>OUT</sub>	I <sub>LED</sub>	
6 to 32 VDC	20V at 1A	20V	1A	

#### 2: Efficiency

	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency
12V	12V	1.87A	20V	1A	88.98%
24V	24V	0.93A	20V	1A	89.51%

ltem	Designation	Description	Part No.	Vendor
1	U1	Buck-boost controller for constant-current LED drivers	LM3423 (eTSSOP-20)	National
2	L1	22 µH	D05040H	Coilcraft
3	C8 (Cin)	330 µF/35V 5 mm Lead	ECA-1VM331	Panasonic
4	C7 (Cout1)	330 µF/35V 5 mm Lead	ECA-1VM331	Panasonic
5	C11 (Cout2)	1210 10 µF, 25V	ECJ-4YB1E106M	Panasonic

#### **Design 3: LED Backlighting Applications Using LM3431**

**Description:** 

#### **LED Backlighting Infotainment**



**LED Backlighting for Dashboards** 



#### **Test Data:**

#### 1: Output Voltage & Current

	Parameter	Reading		
V <sub>IN</sub>	Loading	V <sub>out</sub>	I <sub>LED</sub>	
8 to 18 VDC	4 strings of 8 LEDs, Vf: 3.2V	25.60V	0.14A	

#### 2: Efficiency


	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>LED</sub>	Efficiency
12V	12V	0.34A	25.60V	0.14A	88%

#### **BOM (Main Component)**

ltem	Designation	Description	Part No.	Vendor
1	U1	Boost controller for multi-channel constant-current LED drivers	LM3431 (eTSSOP-28)	National
2	L1	7 μH 3.1A inductor	MSS1038-702NL	Coilcraft
3	C2 (Cin_1)	10 μF 50V electrolytic	UUD1H100MCL	Nichicon
4	C1 (Cin_2)	1 μF 50V B ceramic	GRM32RB11H105KA01	Murata
5	C3 & C8 (Cout)	2 x 4.7 μF 50V X7R ceramic	GRM32ER71H475KA88L	Murata
6	01	60V 200 mA N-channel MOSFET	2N7002K	Vishay
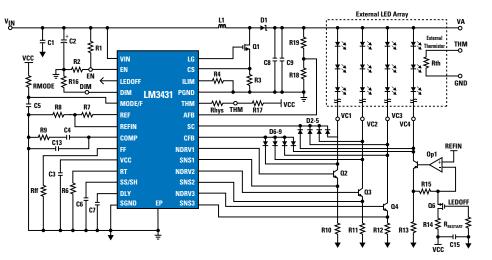
#### V<sub>IN</sub>: 8V to 18V, 4 Strings of 8 LEDs, 140 mA per String

• This circuit is designed to drive four channels of 8 series-connected 140 mA LEDs from a 12V bus battery input for automotive LED backlighting in a TFT display.




#### national.com/LED

## High-Brightness LED Applications TRIAC Dimming
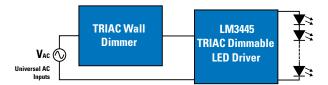
#### TRIAC Dimmable LED Lamp Using LM3445

- The TRIAC phase-control dimmer is today's most popular and common dimming method, but it is designed to interface to a purely resistive load, such as incandescent or halogen light bulbs. Since an LED does not appear as a resistive load to the TRIAC dimmer, dimming an LED using a conventional TRIAC wall dimmer does not achieve good dimming performance.
- National's LM3445 TRIAC dimmable offline LED driver overcomes the issue and enables LEDs to be used as a direct replacement for incandescent or halogen lamp systems which are currently interfaced to a TRIAC wall dimmer. The LM3445 is an offline solution that offers 100:1 full-range, uniform dimming capability, is free of flicker at 100/120 Hz, and supports master/slave operation.



#### Test Data:

#### 1: Output Voltage & Current

Parameter		Reading		
V <sub>IN</sub>	Load	V <sub>OUT</sub>	ILED	
110 VAC	12 LEDs	46 VDC	0.35A	

#### 2: Efficiency

	Reading				
Input Voltage	V <sub>IN</sub>	I <sub>IN</sub>	V <sub>OUT</sub>	I <sub>led</sub>	Efficiency
110 VAC	_	_	46.0V	0.35A	84.20%


#### **BOM (Main Components)**

ltem	Designation	Description	Part No.	Vendor
1	U1	LED driver controller	LM3445MM (mini SOIC-10)	National
2	BR1	Bridge rectifier, SMT, 400V, 800 mA	HD04-T	Diode
3	L2	Inductor. SHLD. SMT, 1A, 470 µH	MSS1260-474KLB	Coilcraft
4	C7, C9	Cap, AL, 200V, 105C, 20%, 33 μF	EKXG201ELL330MK15L	UCC
5	D4, D9	Diode, FR, SOD123, 200V, 1A	RF071M2S	Rohm
6	D10	Diode, FR, SMB, 400V, 1A	MURS140T3G	On Semiconductor
7	01, 02	XSTR, NFET, DPAK, 300V, 4A	FQD7N30TF	Fairchild

#### TRIAC Dimmable LED Lamp with LM3445
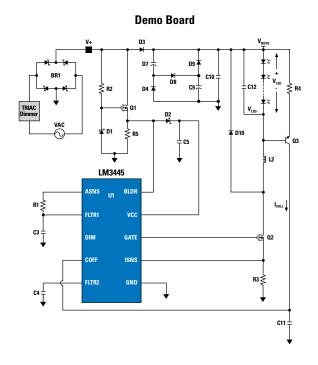
#### **Description:**

• This design is configured to support 90 VAC to 135 VAC inputs to drive 7 or 8 series-connected LEDs at an average current of 350 mA for TRIAC dimmable LED lamp applications.




### Light Matters: The ABC's of LEDs

#### Read Parts 1-4 in full at national.com/led under the Apps tab

When it comes to lighting, it is quite easy to imagine the impact of globally improving the efficiency of lighting sources by 10%. But what if it could be improved by 1000%? The use of newly enhanced LEDs as lighting sources has the potential to achieve these efficiency improvements while maintaining outstanding performance and reliability that supersede many of the currently used sources.

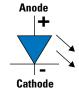**Part 1**, The ABCs of LEDs, sheds some light on the basics of LEDs physical structure, colors, efficiency, applications, and drivers. Learn more about...

- Anatomy
- Color
- Efficiency
- Applications
- Drivers




Many characteristics make buck-based regulators attractive LED drivers. They are simple to configure as a current source and can be realized with minimum component counts, which simplifies the design process, improves the drivers' reliability, and reduces cost. Buck-based LED drivers also provide configuration flexibility since they are compatible with multiple control schemes. They also allow for high-speed dimming as well as wide dimming ranges since they can be configured without output capacitance and are well-matched to various dimming approaches including shunt dimming. All these features make buck-based (step-down) LED drivers the topology of choice whenever the application permits.

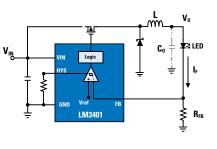**Part 2**, Buck Whenever Possible, discusses why a constantcurrent buck converter should be the first preference when it comes to switch-mode LED drivers. Learn more about...

- Switching Regulators
- Constant-Current Power Stage
- Control-Loop Schemes

What if the application does not permit a buck configuration? Applications such as residential and commercial lighting require thousands of lumens, creating a need to drive LED strings.




The total forward voltage drop of an LED string is equal to the sum of the forward voltage drops of all the LEDs in the string. In some cases, the input voltage range of the system can be lower than the forward voltage drop of the LED string, or it can vary so that sometimes it's lower and sometimes it's higher. These scenarios would require either boost or buck-boost switching regulators.

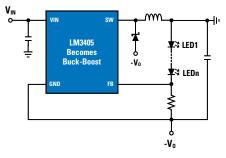**Part 3,** When to Buck and Buck-Boost, investigates larger LED displays and the applications space for other converter topologies. Learn more about...

- Challenges of Boost and Buck-Boost
- Other Topologies


Whether you drive LEDs with a buck, boost, buck-boost, or linear regulator, the common thread is drive circuitry to control the light output. A few applications are as simple as ON and OFF, but a greater number



of applications call for dimming the output between 0 and 100%, often with fine resolution. The designer has two main choices: Adjust the LED current linearly (analog dimming), or use switching circuitry that works at a frequency high enough for the eye to average the light output (digital dimming). Using pulse-width modulation (PWM) to set the period and duty cycle is perhaps the easiest way to accomplish digital dimming, and a buck regulator topology will often provide the best performance.

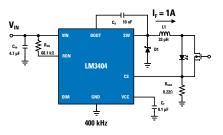**Part 4**, PWM Dimming, describes how to best implement the dimming function. Learn more about...

- PWM Versus Analog Dimming
- Dimming Frequency Versus Contrast Ratio
- Dimming with a Switching Regulator
- Fast PWM with Boost and Buck-Boost



#### national.com/LED

### **Dimming Techniques for Switched-Mode LED Drivers**

The exponential growth of LED lighting has ushered in a vast selection of integrated circuit devices to provide controlled power to LEDs. No longer acceptable to an energy-conscious world, switched-mode LED drivers have long since replaced power-hungry linear current sources as the standard. Applications from flashlights to stadium scoreboards all require precise control of regulated currents. In many instances, real-time changes in LED output intensity are required. This function is commonly referred to as dimming control. This article describes some basic LED theory and several techniques used to provide dimming control to switched-mode LED drivers.

#### **LED Brightness and Color Temperature**

#### **LED Brightness**

The concept of the brightness of visible light from an LED is fairly easy to understand. Assigning a numerical value to the perceived brightness of an LED's output can simply be measured in units of luminous flux density, called candelas (cd). The total power output of an LED is a measurement of the amount of Lumens (Im).

It is also important to understand that average forward LED current determines the brightness of an LED.

**Figure 1** shows the relationship between forward LED current vs. Im output for a certain LED. The relationship is remarkably linear over useable ranges of  $I_F$  or forward current. Note the nonlinearity appearing as  $I_F$  increases. Reduced efficacy in Lumens per Watt arises as the operating current exceeds the linear range. Operation above the linear range results in output power converted to heat from the LED. This wasted heat burdens the LED driver and increases the complexity of the thermal design.

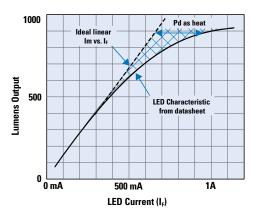


Figure 1. LED Output vs. LED Current

#### **LED Color Temperature**

Color temperature is a metric that describes the color of the LED and is quantified in LED datasheets. The color temperature of a given LED will be specified within a range and will shift with variances in forward current, junction temperature, and age. Lower color temperatures are more red-yellow (called warm) and higher-valued color temperatures are more bluegreen (called cooler). Many colored LEDs will specify dominant wavelength instead of color temperature and are also subject to shift in wavelength.

#### **LED Dimming Methods**

Two popular methods for dimming LEDs in switched-mode driver circuits exist: Pulse-Width Modulation (PWM) dimming and analog dimming. Both methods control the time-averaged current through the LED or LED string, but there are differences between the two which become evident when examining the advantages and disadvantages of the two types of dimming circuits.

**Figure 2** shows a switched-mode LED driver in a buck topology.  $V_{IN}$  must always be higher than the voltage across the LED +  $R_{SNS}$ . The inductor current is the LED current. The current is regulated by monitoring the voltage at the current sense or CS pin. As current sense or CS starts to fall below a set voltage, the duty cycle of the current pulses going through L1, the LED, and  $R_{SNS}$  increase, which increases the average LED current.

#### **Analog Dimming**

Analog dimming of LEDs is the adjustment of cycle-by-cycle LED current. More simply put, it is the adjustment of the constant LED current level. Analog dimming can be accomplished by an adjustment of the current sense resistor  $R_{SNS}$ , or by driving an analog voltage on some DIM function pin of the IC. *Figure 2* shows two examples of analog dimming.

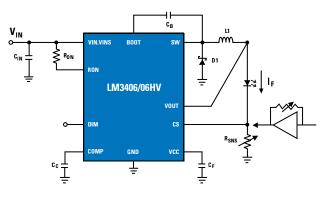


Figure 2. Buck Regulator Topology

#### Analog Dimming by Adjustment of R<sub>SNS</sub>

It is clear from *Figure 2* that a change in value of  $R_{SNS}$  will correspond to a change in LED current with a fixed CS reference voltage. If one could find a potentiometer that could handle the high LED current and also was available in sub-1 Ohm values, this would be a viable method to dim the LED.

Analog Dimming by Driving DC Voltage on the CS Pin

More complex is a technique to directly control the cycle-bycycle current of the LED by means of driving a voltage into the CS pin. The voltage source is typically inserted into a feedback loop where LED current is sampled and buffered by the amplifier (*Figure 2*). The LED current can be controlled by the gain of the amplifier. With this feedback circuitry, functionality such as current and thermal foldback can be implemented for further LED protection.

A disadvantage to analog dimming is that the color temperature of the emitted light can vary as a function of LED current. In situations where the color of the LEDs is critical, or the particular LED exhibits a large change in color temperature with changes in LED current, dimming the output of the LED by changing the LED current would be prohibitive.

#### **PWM Dimming**

The PWM method of dimming is the actual start and restart of the LED current for short periods of time. The frequency of this start-restart cycle must be faster than the human eye can detect to avoid a flickering effect, about 200 Hz or faster is usually acceptable.

The dimming of the LED now becomes proportional to the duty cycle of the dimming waveform, governed by the formula:

$$I_{\text{DIM-LED}} = D_{\text{DIM}} \times I_{\text{LED}}$$

where  $I_{DIM-LED}$  is the average LED current,  $D_{DIM}$  is the duty cycle of the dim waveform, and  $I_{LED}$  is the nominal LED current setup with the selection of  $R_{SNS}$  as shown in *Figure 3*.

#### Modulating the LED Driver

Many modern LED drivers feature a specialized PWM DIM pin that accepts a wide range of PWM frequencies and amplitudes, allowing a simple interface to external logic. The DIM function only shuts down the output drive while leaving the internal circuitry operating, avoiding the delay of restarting the IC. Output Enable pins and other logic shutdown functions can be used.

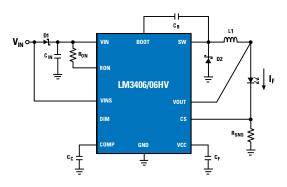


Figure 3. Two-Wire PWM Dimming

#### **Two-Wire PWM Dimming**

Two-wire PWM dimming is a popular method for automotive interior lighting. As  $V_{IN}$  is modulated below 70% of  $V_{IN-NOMINAL}$ , the VINS pin *(Figure 3)* detects the change in voltage and converts the PWM waveform into a corresponding PWM of the output drive. The disadvantage to this method is the power source to the converter must contain a circuit to provide a PWM waveform to its DC output.

#### Fast PWM Dimming with a Shunt Device

Because of the delays in shutdown and start up of the converter's output, there is a limit to the PWM dimming frequency and range of duty cycles. To help overcome this delay, an external shunt device such as the FET shown in Figure 4 can be placed parallel to the LED or LED string to quickly bypass the converter's output current around the LED(s).

The current in the inductor stays continuous during the "LED shutdown time," avoiding the long delay in ramping up and down the inductor current pedestal. The delay time now shifts to the limits of the shunt device's rise and fall times. *Figure 4* shows the LM3406 fitted with a shunt FET and a plot comparing the LED on/off delays between using the DIM function pin vs. the shunt FET. The output capacitance used in both of these measurements is 10 nf and the shunt FET is a Si3458.

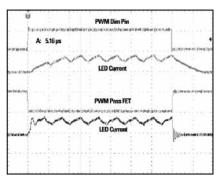


Figure 4. Circuit and PWM Waveforms

#### national.com/LED

### **Designer's Corner**

Caution should be used with shunting the LED current with current-mode converters because of the overshoot in output current when the FET turns on. The LM340x family of LED drivers are controlled on-time converters and will not exhibit this overshoot. Output capacitance across the LEDs should be kept low to maximize on/off/on transition speed.


A disadvantage to the fast-dim circuit vs. shutting down the outputs is loss of efficiency. While the shunt device is on, a power dissipation of V<sub>SHUNT DEVICE</sub> x I<sub>LED</sub> is lost as heat. Use of low R<sub>DS-ON</sub> FETs will minimize this loss of efficiency.

#### LM3409 Multiple Dimming Functions

National Semiconductor's LM3409 is a unique LED driver in that it provides functionality for easy analog and PWM dimming. There are four possible ways to implement LED dimming on this part:

- 1. Analog dim by directly driving the  $I_{\text{ADJ}}$  pin with a voltage source from 0V to 1.24V
- 2. Analog dim by placing a potentiometer between IADJ pin and GND
- 3. PWM dim with the Enable pin
- 4. PWM dim by external shunt FETs

The LM3409 is wired for analog dimming by use of a potentiometer (*Figure 5*). Internal 5  $\mu$ A current source creates a voltage across R<sub>ADJ</sub>, which in turn varies the internal current sense threshold. The I<sub>ADJ</sub> pin can be directly driven with a DC voltage for the same effect.

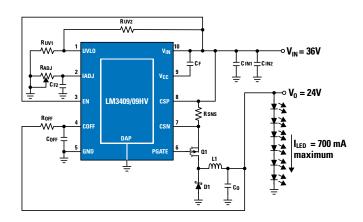

**Figure 5. Analog Dimming Application** 

For an online version, visit: national.com/powerdesigner *Figure 6* shows a plot of measured LED current vs. the potentiometer resistance between the  $I_{ADJ}$  pin to GND. The flattop at 1 Amp represents the maximum nominal LED current, set by the current sense resistor  $R_{SNS}$  shown in *Figure 4*.



Figure 6. LED Current vs. Pot Resistance

**Figure 7** shows the measured LED current as a function of driven DC voltage onto the  $I_{ADJ}$  pin. Notice the same maximum LED current set by  $R_{SNS}$ .

Both analog dimming options are easy to implement and provide very linear dim levels down to around 10% of maximum.

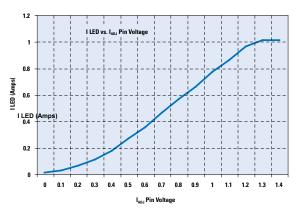


Figure 7. LED vs. I<sub>ADJ</sub> Pin Voltage

#### **Summary**

There are many approaches to dimming LEDs powered by switched-mode regulators. The two main categories, PWM and analog, both have advantages and disadvantages. PWM dimming greatly reduces color changes in the LED with varying brightness levels at the expense of additional logic to create the PWM waveforms. Analog dimming can be a more simplistic circuit, but may be inappropriate for applications that require a constant color temperature.

### WEBENCH® LED Designer

### WEBENCH® LED Tool for the Optimal LED and a Complete Power Supply Design in Minutes

#### 1. Choose an LED at national.com/led

Enter your requirements and receive a list of LEDs from the leading manufacturers

#### 2. Design Your Power Supply

Select a PowerWise® LED driver from the optimized short list provided

#### 3. Complete Your Design

Optimize between efficiency and size

#### 4. Verify Your Design

Use the electrical simulator to verify circuit stability and operation


#### 5. Order a Customized Prototype Kit

Guaranteed to ship in just one business day
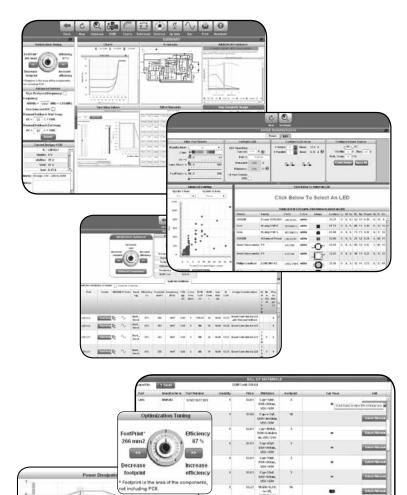
#### Watch Analog by Design

"Driving High-Power LEDs Without Getting Burned" www.national.com/analog/nationalTV

Try the WEBENCH LED Designer tool today at: national.com/LED



8 **4** 

28 38 48 58 LEO Temperature (

📕 Din Pd 📗

D

all pressore

100

### **Design Tools**

**Resources for Next-Generation Design** 

### WEBENCH®

Design, build, and test analog circuits in this online design and prototyping environment.

#### national.com/webench



Register to receive updates on the products and technical topics that interest you—spam-free!

#### national.com/newsletter



Browse and watch product videos in National's video center.

#### national.com/videos



Expand your knowledge and understanding of analog with our free educational online seminars.

#### national.com/training



Published bi-monthly, the Power Designer technical articles cover key power design tips and techniques for today's design engineers.

#### national.com/powerdesigner



Published bi-monthly, the Signal Path Designer technical articles cover analog signal path tips and techniques for today's design engineers.

#### national.com/spdesigner



National's monthly analog design technical journal.

national.com/edge

#### KNOWLEDGE Base

Easy, natural-language online search engine provides quick access to products and technical information.

#### national.com/kbase



Tune in to learn technical energy-saving tips, hosted by National's PowerWise® Technologist, Richard Zarr, and streamed 24/7 on the web.

national.com/powerwisetv

#### **Tools for Energy-Efficient Designs**

Access white papers, reference designs, and application notes on PowerWise® products and systems. national.com/powerwise

#### **Parametric Catalog and Search**

Search for desired product folder, product database by attributes of interest.

#### **Application Solutions**

Access over 100 dynamic diagrams for medical systems, consumer electronics, communications, and many more applications. national.com/solutions

#### **Application Notes**

Access hundreds of application notes on a variety of design topics from product to end application specific app notes. **national.com/appnotes** 

#### **FPGA** Design Guides

These design guides feature National device solutions by part number for different FPGA manufacturers, including Xilinx and Altera. national.com/guides

#### **Document Library**

Find end market solutions and products using National's Solutions Guides. national.com/guides



# **Best-in-Class Dimming Performance. High Efficiency.**

#### High-Performance, TRIAC Dimmable LED Driver

National's industry-leading TRIAC dimmable offline LED driver solution is perfect for any application where an LED driver must interface to a standard TRIAC wall dimmer. National's new TRIAC dimmable LED driver delivers a wide, uniform dimming range free of flicker, best-in-class dimming performance, and high efficiency—all while maintaining ENERGY STAR® power factor requirements in a typical application.

- ✔ Online design tools
- V Reference designs
- ✓ Application notes



Full Range Dimming Capability National's TRIAC dimmable LED driver offers 100:1 full range dimming capability, going from full light to nearly imperceptible light in a continuous range without being extinguished, and maintains a constant current to large strings of LEDs driven in series off of a standard line voltage.

#### Easy To Use

National's TRIAC dimmable LED driver enables a direct replacement of incandescent or halogen lamp systems that are currently interfaced to a TRIAC dimmer without having to change the original infrastructure or sacrifice performance. In addition, the new TRIAC dimmable LED driver is available in WEBENCH® LED Designer to allow for easy and quick design in.

#### Uniform Dimming Without Flicker

National's TRIAC dimmable LED driver allows master-slave operation control in multi-chip solutions which enables a single TRIAC dimmer to control multiple strings of LEDs with smooth consistent dimming, free of flicker.



### Worldwide Design Centers and Manufacturing Facilities



#### **Design Centers**

#### USA:

Chandler, Arizona Federal Way, Washington Fort Collins, Colorado Grass Valley, California Indianapolis, Indiana Longmont, Colorado Norcross, Georgia Phoenix, Arizona Salem, New Hampshire Santa Clara, California South Portland, Maine Tucson, Arizona

#### EUROPE:

Delft, Netherlands Eindhoven, Netherlands Greenock, Scotland Milan, Italy Oulu, Finland Tallinn, Estonia Unterhaching, Germany

#### ASIA:

Bangalore, India Hong Kong, China

#### **Manufacturing Facilities**

Wafer (Die) Fabrication: Arlington, Texas South Portland, Maine Greenock, Scotland

Chip Test and Assembly: Melaka, Malaysia

#### World Headquarters

2900 Semiconductor Drive Santa Clara, CA 95051 USA +1 408 721 5000 www.national.com Mailing Address: PO Box 58090 Santa Clara, CA 95052 support@nsc.com European Headquarters Livry-Gargan-Str. 10 82256 Fürstenfeldbruck Germany +49 8141 35 0 europe.support@nsc.com Asia Pacific Headquarters 2501 Miramar Tower 1 Kimberley Road Tsimshatsui, Kowloon Hong Kong +852 2737 1800 ap.support@nsc.com Japan Headquarters Beside KIBA 2-17-16 Kiba, Koto-ku Tokyo, 135-0042, Japan +81 3 5639 7300 jpn.feedback@nsc.com



© National Semiconductor Corporation, June 2010. National Semiconductor, 🖒 LLP, Power/Vise, and WEBENCH are registered trademarks of National Semiconductor Corporation. All other brands or product names are trademarks of registered trademarks of their respective holders. All rights reserved.